

Bihar Engineering University, Patna

B.Tech 3rd Semester Examination, 2024

Course: B.Tech
Code: 100306

Subject: Electrical Circuit Analysis

Time: 03 Hours
Full Marks: 70

Instructions: -

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

Q.1 Choose the correct answer from the following (Any seven question only):

[2 x 7 = 14]

- (a) Thevenin's and Norton's equivalents are:
 - (i) ~~different representations with different values~~
 - (ii) Identical in all circuits
 - (iii) Equivalent with same behavior at load terminals
 - (iv) Applicable only for AC circuits
- (b) Mesh analysis is preferred when:
 - (i) ~~The number of meshes is more than nodes~~
 - (ii) The number of meshes is less than nodes
 - (iii) Dependent sources are present
 - (iv) Circuits are complex
- (c) The steady-state response in a circuit is observed:
 - (i) During initial $t = 0$
 - (ii) ~~When $t \rightarrow \infty$~~
 - (iii) When energy is maximum
 - (iv) Just after switching
- (d) In a critically damped RLC circuit, the roots of characteristic equation are:
 - (i) Complex conjugates
 - (ii) ~~Real and distinct~~
 - (iii) Real and equal
 - (iv) Purely imaginary
- (e) The admittance of an inductor is:
 - (i) $j\omega L$
 - (ii) $1/(j\omega L)$
 - (iii) $-j\omega L$
 - (iv) ~~$j\omega C$~~
- (f) The average power in a purely capacitive circuit is:
 - (i) ~~Zero~~
 - (ii) Maximum
 - (iii) Depends on frequency
 - (iv) Infinite
- (g) Poles are values of 's' where:
 - (i) Input is zero
 - (ii) Output is zero
 - (iii) ~~Denominator of transfer function is zero~~
 - (iv) Numerator is zero
- (h) Convolution in time domain becomes.....in Laplace domain:
 - (i) Division
 - (ii) Addition
 - (iii) Multiplication
 - (iv) Integration
- (i) A network is reciprocal if it contains only:
 - (i) Resistors
 - (ii) Resistors and capacitors
 - (iii) ~~Passive linear elements~~
 - (iv) Active devices
- (j) The h-parameters are mainly used for:
 - (i) Filter design
 - (ii) Inductor modeling
 - (iii) ~~Transistor modeling~~
 - (iv) Transformer design

- Q.2 (a) State Maximum Power Transfer Theorem. Prove that efficiency of the circuit under maximum power transfer condition is 50%. [7]
- (b) Find the voltage across 3Ω resistor using any theorem for the circuit shown in Figure-1 [7]

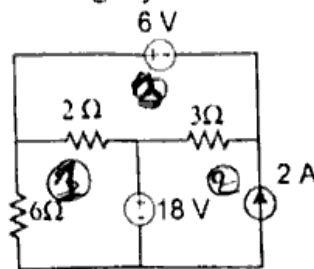


Figure 1

- Q.3 (a) Find V_A using the principle of superposition in network as shown in Figure 2. [7]

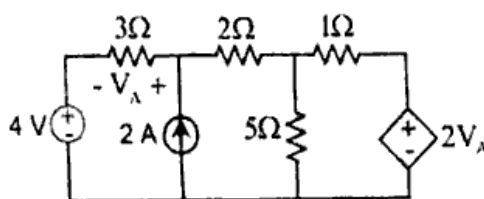


Figure 2

- (b) State Reciprocity Theorem. Verify the Reciprocity Theorem for the circuit shown in Figure 3. [7]

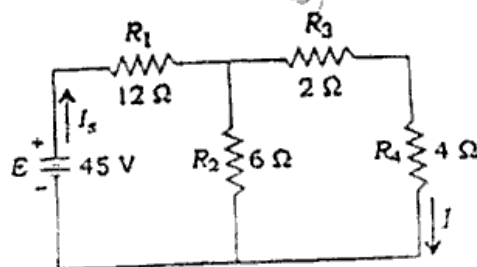


Figure 3

- Q.4 (a) Explain the behaviour of RL and RC elements for transient condition. Mention their representation at the time of switching. [7]
- (b) Draw the circuit of parallel RLC circuit and derive the formulae for resonant frequency, half-power frequencies, bandwidth and quality factor. [7]
- Q.5 (a) Determine Laplace transform of a following (i) $\sin 2t$ (ii) $\cos 2t$ [7]
- (b) Synthesis the waveform shown in Figure 4 below and Determine Laplace transform of periodic waveform. [7]

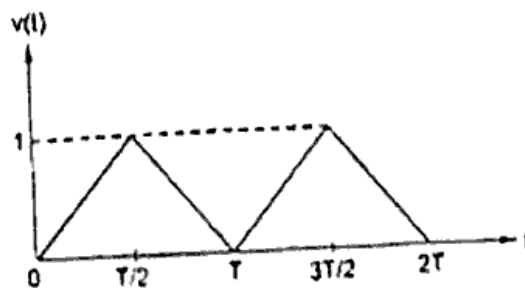


Figure 4

- Q.6 (a) To find Thevenin equivalent between terminals 'a' and 'b' as shown in Figure 5. [7]

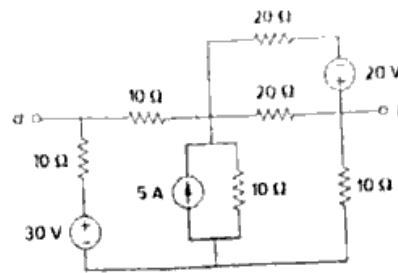


Figure 5

- (b) A switch is moved from position 1 to 2 at $t=0$ as shown in Figure 6. Find $V_R(t)$ and $V_C(t)$ for $t>0$. [7]

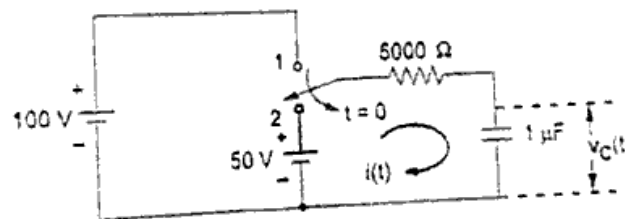


Figure 6

- Q.7 (a) Explain about the transmission parameters and derive the condition for symmetry and reciprocity. [7]
(b) Determine z-parameter of network shown below in Figure 7 & give its equivalent circuit. [7]

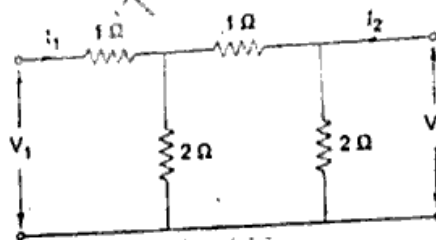


Figure 7

- Q.8 (a) Define two-port network and write assumptions to be made to find network and also obtain Y parameter. [7]
(b) Two coils connected in series have an equivalent inductance of 10H. When the connections of one coil are reversed, the effective inductance is 6H. If the coefficient of coupling is 0.6, calculate the self-inductance of each coil and mutual inductance. [7]

- Q.9 Write short notes on any two of the following: [7 x 2 = 14]

- Poles and Zeros
- Convolution integral
- Mutual coupled circuits
- Transmission and Hybrid parameters